

CCPS213 Lab BiG 4 (10%) Due: Dec 7th @23:00

Part A) Q1(70 Marks):

Decoders can be regarded as a kind of Converters.

From The truth table convert the BCD to 7 segment to specified output functions: H,T,L,K,M,L,N

- Simplify the output function using Kmap (SOP or POS which ever is more direct).
Make sure to use the "DON'T CARE" conditions as part of map.
- Draw a circuit for each of your simplified functions in the simulator. Attach switches for inputs, and light bulbs for outputs (or 7 segment led).
- Attach led to each output of the function

	BCD(8421)	OUTPUTS
<i>DEC</i>	<i>A B C D</i>	<i>H I J K L M N</i>
0	0 0 0 0	1 1 1 1 1 0
1	0 0 0 1	0 1 1 0 0 0
2	0 0 1 0	1 1 0 1 1 0 1
3	0 0 1 1	1 1 1 1 0 0 1
4	0 1 0 0	0 1 1 0 0 1 1
5	0 1 0 1	1 0 1 1 0 1 1
6	0 1 1 0	1 0 1 1 1 1 1
7	0 1 1 1	1 1 1 0 0 0 0
8	1 0 0 0	1 1 1 1 1 1 1
9	1 0 0 1	1 1 1 1 0 1 1
10	1 0 1 0	x x x x x x x
11	1 0 1 1	x x x x x x x
12	1 1 0 0	x x x x x x x
13	1 1 0 1	x x x x x x x
14	1 1 1 0	x x x x x x x
15	1 1 1 1	x x x x x x x


Part B) (130 marks)

Design a circuit which take in 2 sets of 4bits and add them together, display resulting sum value as decimal digit(s) on 2 seven segments led. To display the binary sum (c+4bits) on 2 seven segments led you may have to custom design a new converter, or create one using 2 adders along with gates.

Draw circuit using Logisim. Make sure to add input switch for the 4 X_i and Y_i .

To get full marks your circuit must be able to display from the min to max range of adding 2 set of 4 bits.

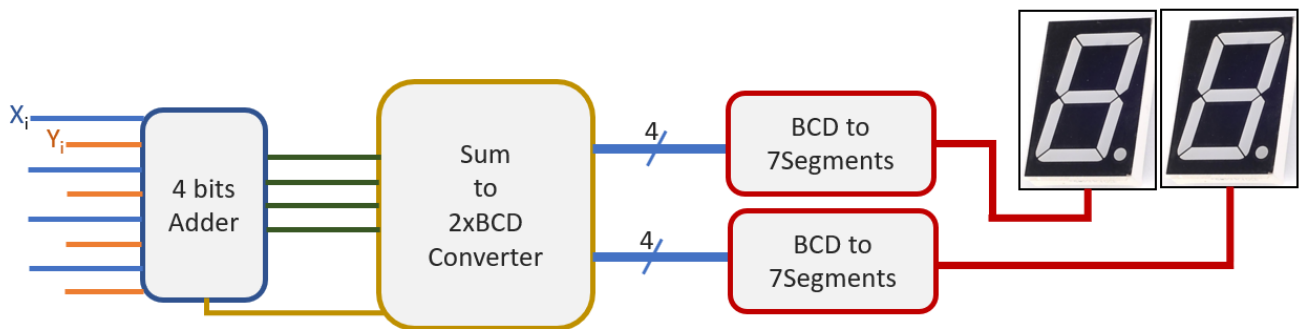You may use prebuilt adder from Logisim or from your prior works. You may use your BCD to 7 segment circuit from part A or the one provided to you on Dec 3rd.



Make to show all your works for part A & B.

Submit: one document showing you derivations and one circuit file with all your circuits

Hint for part B converter: look at decay counter detection gate for the one with using adders,

And for custom design think '5-8' converter: self investigate >4 literals kmap

Binary sum (c +4 bits)	BCD (2x4)
.	.
.	.
.	.