

Andy Lee – 500163559

Lab 4

Part A

	BCD(8421)	OUTPUTS						
Dec.	ABCD	H	I	J	K	L	M	N
0	0000	1	1	1	1	1	1	0
1	0001	0	1	1	0	0	0	0
2	0010	1	1	0	1	1	0	1
3	0011	1	1	1	1	0	0	1
4	0100	0	1	1	0	0	1	1
5	0101	1	0	1	1	0	1	1
6	0110	1	0	1	1	1	1	1
7	0111	1	1	1	0	0	0	0
8	1000	1	1	1	1	1	1	1
9	1001	1	1	1	1	0	1	1
10	1010	x	x	x	x	x	x	x
11	1011	x	x	x	x	x	x	x
12	1100	x	x	x	x	x	x	x
13	1101	x	x	x	x	x	x	x
14	1110	x	x	x	x	x	x	x
15	1111	x	x	x	x	x	x	x

$$H = A'B'C'D' + A'B'CD' + A'B'CD + A'BC'D + A'BCD' + A'BCD + AB'C'D' + AB'C'D$$

$$I = A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + A'BC'D' + A'BCD + AB'C'D' + AB'C'D$$


$$J = A'B'C'D' + A'B'C'D + A'B'CD + A'BC'D' + A'BC'D + A'BCD' + A'BCD + AB'C'D' + AB'C'D$$

$$K = A'B'C'D' + A'B'CD' + A'B'CD + A'BC'D + A'BCD' + AB'C'D' + AB'C'D$$

$$L = A'B'C'D' + A'B'CD' + A'BCD' + AB'C'D'$$







$$M = A'B'C'D' + A'BC'D' + A'BC'D + A'BCD' + AB'C'D' + AB'C'D$$
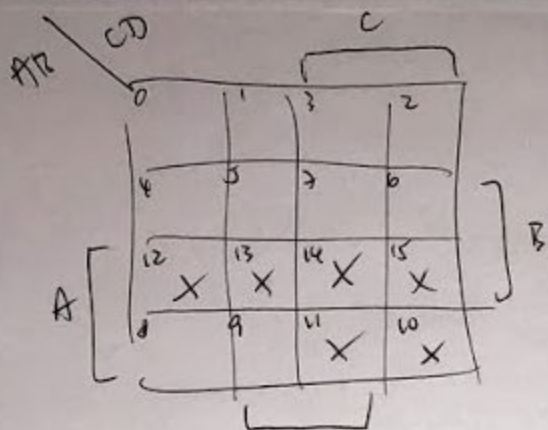
$$N = A'B'CD' + A'B'CD + A'BC'D' + A'BC'D + A'BCD' + AB'C'D' + AB'C'D$$



$$X = \overline{A} \overline{B} \overline{C} \overline{D}$$

A	B	C	D
1	0	0	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

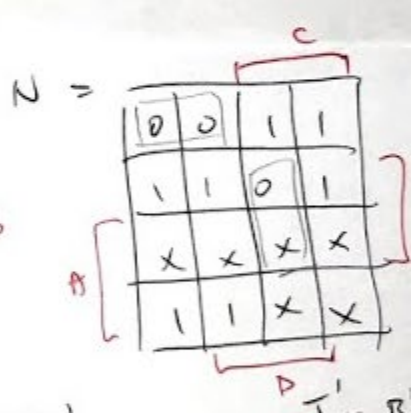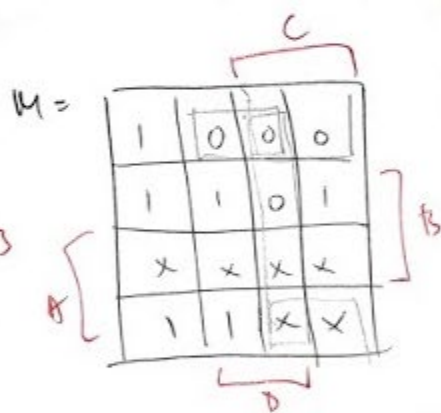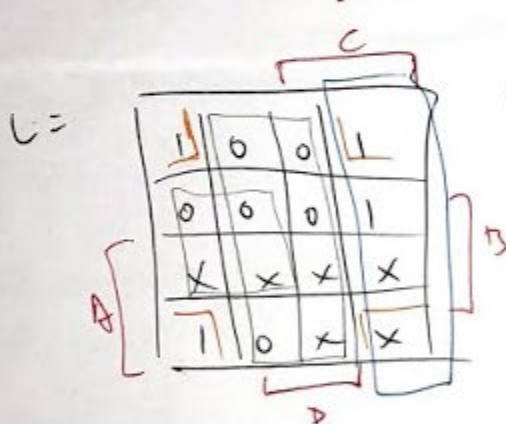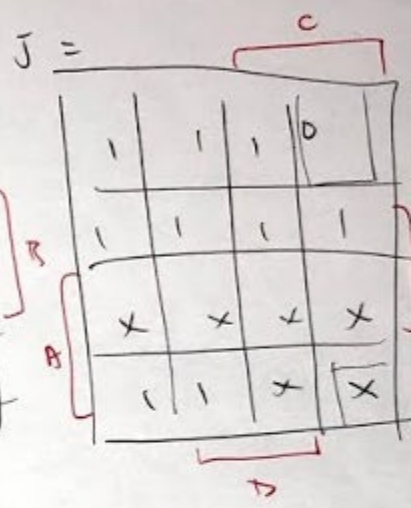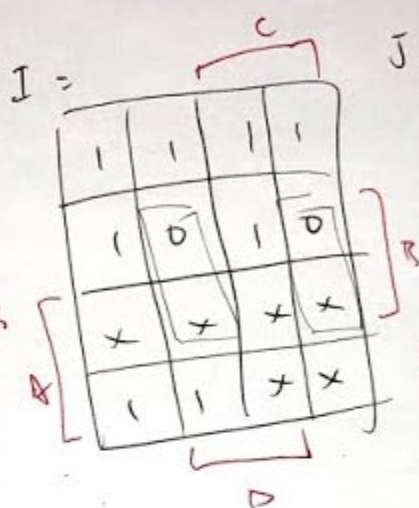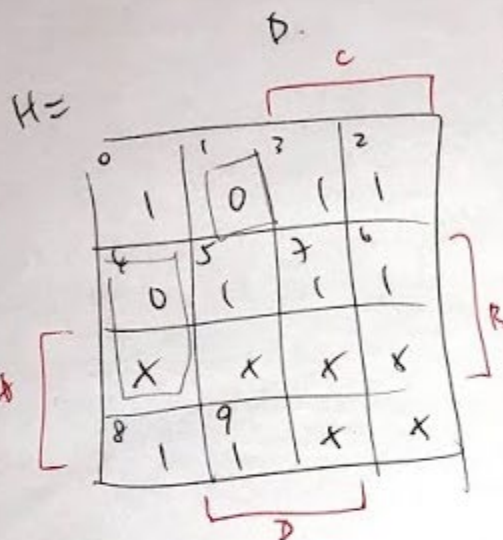

$$H' = A'B'C'D + BC'D'$$

$$H = \overline{(A'B'C'D + BC'D')}$$

$$(H') = (A'B'C'D + BC'D')$$

$$H = \overline{(A'B'C'D)} \overline{(BC'D')}$$

$$= (A+B+C+D)(B'+C+D)$$

$$I' = BC'D + BCD'$$

$$(I') = (BC'D + BCD')$$

$$= \overline{(BC'D)} \overline{(BCD')}$$

$$= (\overline{B} + \overline{C} + \overline{D})(\overline{B} + \overline{C} + \overline{D})$$

$$J' = B$$

$$(J') = (\overline{B})$$

$$J = B$$

$$L' = D + BC'$$


$$L = \overline{(D + BC')} = (\overline{D})(\overline{BC'})$$

$$M' = CD + \overline{C}D'$$

$$M = \overline{(CD + \overline{C}D')} = (\overline{CD})(\overline{\overline{C}D'}) = (\overline{C} + \overline{D})(C + D)$$

$$\begin{aligned}
H &= (A + B + C + D')(B' + C + D) \\
I &= (B' + C + D')(B' + C' + D) \\
J &= (B + C' + D) \\
K &= (B' + C + D)(B' + C' + D')(A + B + C + D') \\
L &= (D')(B' + C) \\
M &= (C' + D')(A + B + D')(B + C') \\
N &= (A + B + C)(B' + C' + D')
\end{aligned}$$

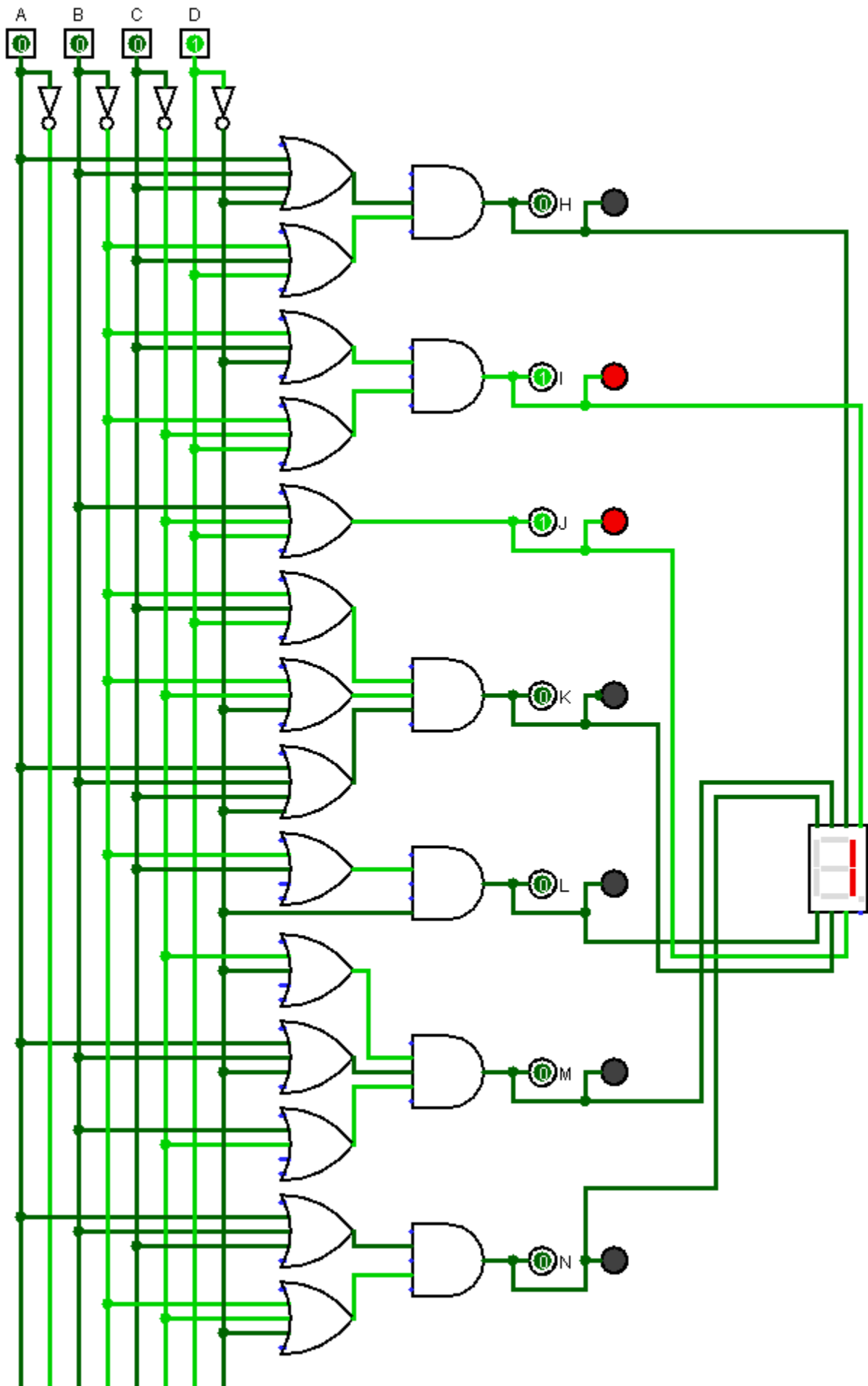Using the above we've built BCD decoder and turn it into a component



Part B solution in Logism file.

Utilizing components *full adder* from lab 3, *BCD-decoder* from this lab Part A, *4bit-to-BCD converter*, the final circuit named *Part2-final*.

